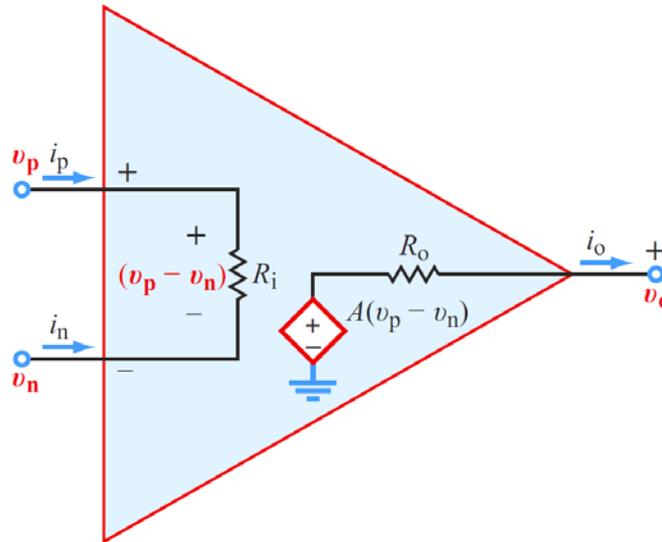


## Open loop amplifier model and parameters

The operational amplifiers used in this class can be modeled for many practical applications, with a linear circuit. That is to say, we can use linear elements we've already learned about to build a simple model of how an amplifier would respond to changes in currents and voltages.



- In the model above,  $v_p$  and  $v_n$  are referred to as the non-inverting and inverting terminals, respectively.  $R_i$  and  $R_o$  are the input and output resistances, respectively.
- In an ideal amplifier,  $R_i$  is infinite (that is, the input is an open circuit);  $R_o = 0 \Omega$  (that is, the voltage source is shorted directly to  $v_o$ ) and  $A$  is infinite (more on this soon).
- In typical op-amps,  $R_i > 10^8 \Omega$ ,  $R_o < 10 \Omega$ ,  $A > 10^6 \text{ V/V}$ .
- The *power rails* (the two terminals through which op amps receive power from an external supply) are not shown in the model above. Sometimes they are drawn into the figure.
- The positive rail (historically labelled  $V_{DD}$  or  $V_{CC}$ ) sets the highest voltage the amplifier can output (under any condition).
- The negative rail (historically labelled  $V_{SS}$  or  $V_{EE}$ ) sets the lowest voltage the amplifier can output (under any condition).

### The Comparator

Notice that if  $A$  is very high, the open loop amplifier above will likely be *railed*. That is, its output will be either  $V_{DD}$  or  $V_{SS}$ . Why? Consider an amplifier with an  $A$  of  $10^6 \text{ V/V}$ ,  $V_{DD} = 10 \text{ V}$  and  $V_{SS} = -10 \text{ V}$ . For simplicity, assume  $R_i$  is infinite and  $R_o$  is  $0 \Omega$ . For any input where  $v_p - v_n > 10 \mu\text{V}$ , the output will be  $10 \text{ V}$ . Conversely, for any input where  $v_p - v_n < -10 \mu\text{V}$ , the output will be  $-10 \text{ V}$ . This means for any reasonable input voltage difference, the output will either be  $10 \text{ V}$  or  $-10 \text{ V}$  (there is a very narrow range, between  $-10 \mu\text{V}$  and  $10 \mu\text{V}$ , where the output is exactly  $A*(v_p - v_n)$  but it is negligible; the larger this  $A$ , the smaller this linear range is). In this mode, the amplifier acts as a comparator; that is, it compares the inputs: if  $v_p$  is larger than  $v_n$ , it outputs  $V_{DD}$ ; if  $v_n$  is larger than  $v_p$ , it outputs  $V_{SS}$ .