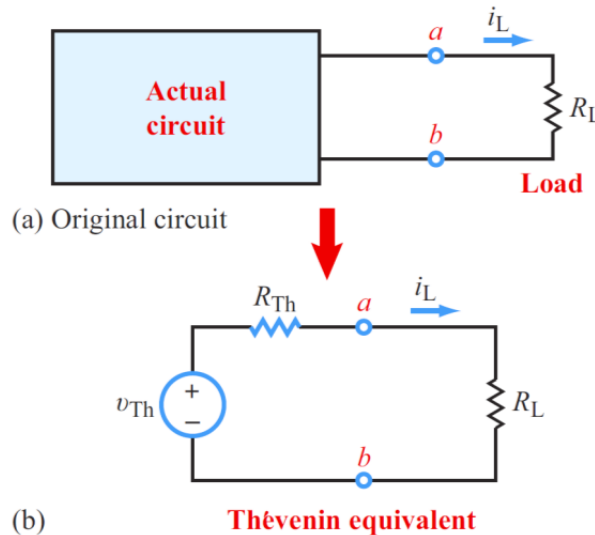


# Thévenin Equivalent Circuits

In the 1880s, a French engineer named Leon Thévenin introduced the concept known today as Thévenin's theorem, which asserts:

A linear circuit can be represented at its output terminals by an equivalent circuit consisting of a series combination of a voltage source  $v_{Th}$  and a resistor  $R_{Th}$ , where  $v_{Th}$  is the open-circuit voltage at those terminals (no load) and  $R_{Th}$  is the equivalent resistance between the same terminals when all independent sources in the circuit have been deactivated.





*A circuit can be represented in terms of a Thévenin equivalent comprised of a voltage source  $v_{Th}$  in series with a resistance  $R_{Th}$ .*

There are several methods for obtaining the Thévenin equivalent components,  $v_{Th}$  and  $R_{Th}$ , given a linear circuit. Most introductory circuits textbooks discuss the various methods and their application.

One basic method is as follows:

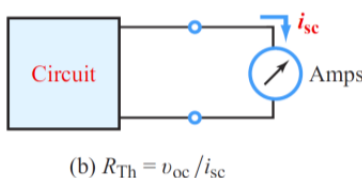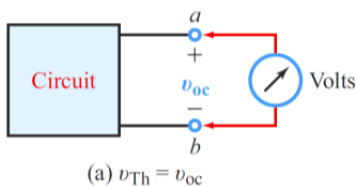- The Thévenin voltage  $v_{Th}$  is obtained by removing the load  $R_L$  (replacing it with an open circuit), and then measuring or computing the open-circuit voltage at the same terminals.
- The short-circuit current is obtained by replacing the load with a short circuit and then measuring or computing the short circuit current flowing through it.



The Thévenin voltage is equal to the open-circuit voltage and Thévenin resistance is equal to the ratio of  $v_{oc}$  to  $i_{sc}$ , where  $i_{sc}$  is the short-circuit current between the output terminals.